

### Answer on Question #66378-Physics-Mechanics-Relativity

An emf of 100 V is applied to a series RC circuit in which the resistance is 200 ohms and the capacitance is  $10^{-4}$  farads. Determine the charge  $q(t)$  on the capacitor if  $q(0) = 0$ . Also determine the current  $i(t)$ .

#### Solution

The charge on capacitor is

$$q(t) = Q \left( 1 - e^{-\frac{t}{\tau}} \right).$$

$$\tau = RC = (200)(10^{-4}) = 0.02 \text{ s.}$$

$$Q = CE = (10^{-4})(100) = 0.01 \text{ C.}$$

Thus,

$$q(t) = 0.01(1 - e^{-50t}) \text{ C.}$$

The current is

$$i(t) = I e^{-\frac{t}{\tau}}.$$

$$I = \frac{Q}{\tau} = \frac{0.01}{0.02} = 0.5 \text{ A.}$$

Thus,

$$i(t) = 0.5e^{-50t} \text{ A.}$$

Answer provided by <https://www.AssignmentExpert.com>