

## Answer on Question # 69009, Physics - Electric Circuits

**Question:** How to calculate the current if the capacitance and the voltage are given?

**Solution:** Suppose, capacitance of the capacitor =  $C$ , voltage =  $V$  and charge =  $Q$ .

Then we know, Charge ( $Q$ ) = Capacitance ( $C$ ) x Voltage ( $V$ ).

The current ( $I$ ) flowing into the capacitor is the rate of change of the charge across the capacitor plates,  $I = \frac{dQ}{dt} = C \frac{dV}{dt}$ .

where,  $dt$  = change of time. & capacitance value ( $C$ ) is constant.

**Answer:** The current-voltage relationship of a capacitor is  $I = C \frac{dV}{dt}$ .

Answer provided by <https://www.AssignmentExpert.com>