

Answer on Question #69407-Physics-Other

In an LCR circuit, $L = 2 \text{ mH}$, $C = 5 \mu\text{F}$ and

$R = 40 \text{ Ohm}$ comment on the nature of damping.

Solution

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \cdot 10^{-3})(5 \cdot 10^{-6})}} = 10^4 \frac{\text{rad}}{\text{s}}$$

$$\alpha = \frac{R}{2L} = \frac{40}{2(2 \cdot 10^{-3})} = 10^4 \frac{\text{rad}}{\text{s}}$$

$$\alpha = \omega_0$$

Thus, this circuit is **critically-damped**.

Answer provided by AssignmentExpert.com