

## Answer on Question #69488, Physics / Electric Circuits

h-parameters of a single stage CE amplifier are given as  $h_{ie} = 1 \text{ kW}$ ,  $h_{re} = 3 \times 10^{-4}$ ,  $h_{fe} = 60$  and  $h_{oe} = 25 \mu\text{A/V}$ .

Calculate  $A_i$ ,  $A_v$  and  $Z_{out}$  with  $R_s = 100\text{W}$  and  $R_L = 10\text{kW}$ .

**Solution.**

$$A_i = \frac{-h_{fe}}{1 + h_{oe}R_L} = \frac{-60}{1 + 25 \cdot 10 \cdot 10^3} = -2.4 \cdot 10^{-4}$$

$$A_v = \frac{A_i R_L}{R_i}$$

$$R_i = \frac{-h_{fe} R_L}{R_s + h_{ie}}$$

$$R_i = \frac{-60 \cdot 10 \cdot 10^3}{100 + 1000} = -54.5 \text{ W}$$

$$A_v = \frac{-2.4 \cdot 10^{-4} \cdot 10 \cdot 10^3}{-54.5} = 0.044$$

$$Z_{out} = \frac{1}{h_{oe} - \frac{h_{re}h_{fe}}{h_{ie}}} = \frac{1}{25 - \frac{3 \cdot 10^{-4} \cdot 60}{1000}} = 0.04 \Omega$$

Answer provided by AssignmentExpert.com