


## Answer to Question #69492, Physics / Electric Circuits

### Question:

Design and draw the circuit of a three channel op-amp adder with channel gains of  $-5$ ,  $-10$  and  $-15$  respectively.
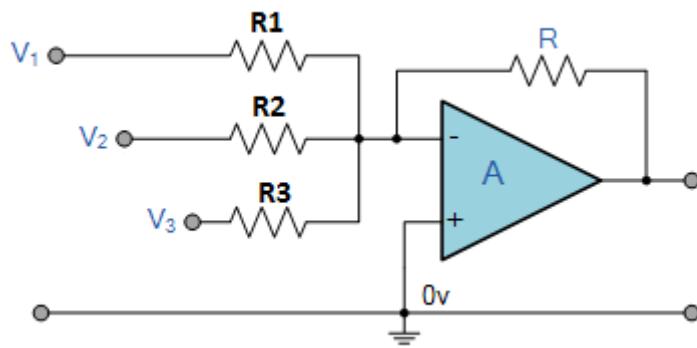
### Solution:

Basically a three channel op-amp adder with channel different gains for each channel is a scaling summing amplifier with a circuit like this



Where

$$R1 = \frac{R}{5}$$

$$R2 = \frac{R}{10}$$

$$R3 = \frac{R}{15}$$