

### Answer on Question #71519, Physics / Electric Circuits

**Question.** A capacitor of capacitance  $100 \mu F$  & a resistance of  $100 \text{ ohm}$  is connected in series with AC supply of  $220 V, 50 Hz$ . The current leads the voltage by????

**Given.**

$C = 100 \mu F$  ;  $R = 100 \text{ ohm}$  ;  $u = 220 V$  ;  $\nu = 50 Hz$  ;  $L = 0$ .

**Find.**

$\varphi$ —?.

**Solution.**

For an AC circuit


$$\operatorname{tg} \varphi = \frac{\omega L - \frac{1}{\omega C}}{R}.$$

We get

$$\operatorname{tg} \varphi = \frac{\omega L - \frac{1}{\omega C}}{R} = \frac{0 - \frac{1}{2 \cdot \pi \cdot \nu \cdot C}}{R} = -\frac{1}{2 \cdot \pi \cdot \nu \cdot C \cdot R} = -\frac{1}{2 \cdot 3.14 \cdot 50 \cdot 100 \cdot 10^{-6} \cdot 100} = -0.31847.$$

So

$$\varphi = -17.66^\circ.$$

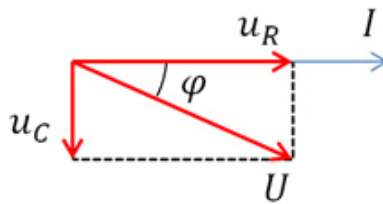

**Answer.** The current leads the voltage by  $17.66^\circ$

Answer provided by <https://www.AssignmentExpert.com>