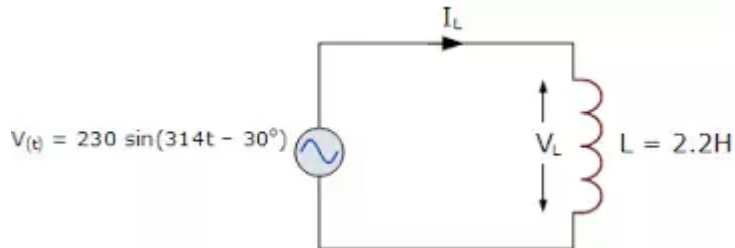


### Answer on Question #73360-Physics-Electromagnetism

Can the end in a conductor be in the same sense as the emf of the source which gives the inductor its magnetic energy?

#### Answer

If any voltage source is connected across any inductor the voltage across the source and inductor will always be the same. Below  $v(t) = V_L$ .



If the source were DC the inductor would just melt due to the high current passing through it as  $V_L = 0$  in steady state. That is why one never connects an inductor across any DC source without resistance to limit the current in steady state. With AC this is not as problematic.

Answer provided by <https://www.AssignmentExpert.com>