

### Answer on Question #73361, Physics / Optics

**Question.** Could the alternating current resistance of a device depends on the frequency?

**Answer.** In general, if the device contains inductance and capacitance the alternating current resistance of a device depends on the frequency as

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2},$$

where  $Z$  is the resistance of a device (impedance);  $R$  – is the resistance;  $L$  – is the inductance of a device;  $C$  – is the capacitance of a device and  $\omega = 2\pi\nu$  – is the angular frequency ( $\nu$  is the signal frequency).

Answer provided by <https://www.AssignmentExpert.com>