

### Answer on Question #74366 Physics / Other

A  $C = 2\mu\text{F}$  capacitor charged originally to a potential difference of  $V_0 = 60\text{V}$  is discharged across a  $R = 22\text{m}\Omega$  resistor as shown in the figure. Calculate the time constant of the circuit and the potential difference across the capacitor after this time constant time?

**Solution:**

The time constant

$$\tau = RC = 22 \times 10^{-3} \times 2 \times 10^{-6} = 44 \times 10^{-9} \text{ s}$$

The potential difference across the capacitor as a function of time

$$V(t) = V_0 e^{-\frac{t}{\tau}}$$

So

$$V(\tau) = V_0 e^{-1} = 60 \times e^{-1} = 22 \text{ V}$$

**Answers:**  $44 \times 10^{-9} \text{ s}$ ,  $22 \text{ V}$

Answer provided by <https://www.AssignmentExpert.com>