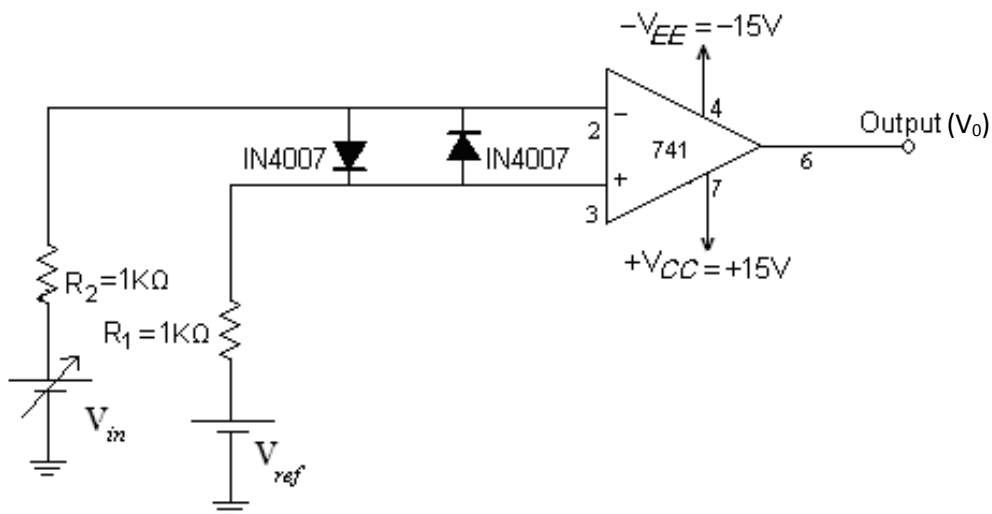


Answer on Question #77119, Physics -Electric Circuits:

Question: Design and draw a voltage comparator circuit using op-amp IC 741 to give $+V_{\text{Sat}}$ at the output if the input voltage is less than -3V and $-V_{\text{Sat}}$ for input more than -3V .

Solution:



Design: A fixed reference voltage V_{ref} and varying voltage V_{in} is applied as shown in Fig. Vary the input voltage above and below the V_{ref} and note down the output at pin 6 (V_o) of 741 IC.

Two Diodes IN 4007 are there for protection purpose.

Observe that, when V_{in} is less than $V_{\text{ref}} = -3\text{V}$, Output voltage V_o is $+V_{\text{Sat}} (= +V_{\text{CC}})$.

And when V_{in} is greater than $V_{\text{ref}} = -3\text{V}$, Output voltage V_o is $-V_{\text{Sat}} (-V_{\text{EE}})$.

Answer: Inverting comparator circuit.

Answer provided by <https://www.AssignmentExpert.com>