

### Answer on Question # 78097, Physics -Electric Circuits:

**Question:** A battery of 10 Volts is connected to a resistance of 20 ohms through a variable resistance R. The amount of charge which has passed in the circuit in 4 minutes, if the variable resistance R is increasing at the rate of 5 ohms/min , will be ?

**Solution:**  $I = \frac{dq}{dt} = \frac{V}{R}$  [I = current, V = voltage, R = resistance, dq = change in charge and dt = change in time.]

$$\text{Now, } \frac{dq}{dt} = \frac{dq}{dR} \cdot \frac{dR}{dt}$$

$$\text{And } \frac{dR}{dt} = 5 \text{ ohms/min} = \frac{1}{12} \text{ ohms/sec.}$$

$$\text{So, } \frac{dq}{dR} \cdot \frac{dR}{dt} = \frac{V}{R}$$

$$\text{Now, } dq = 12 \times V \times \frac{dR}{R} \quad \left[ \text{As } \frac{dR}{dt} = \frac{1}{12} \right]$$

$$\text{So, } q = 12 \times 10 \int_{20}^{40} \frac{dR}{R}$$

$$= 120. \log 2 \text{ Coulomb.}$$

$$= 83.18 \text{ Coulomb.}$$

**Answer:** So, charge will be 83.18 Coulomb.

Answer provided by <https://www.AssignmentExpert.com>