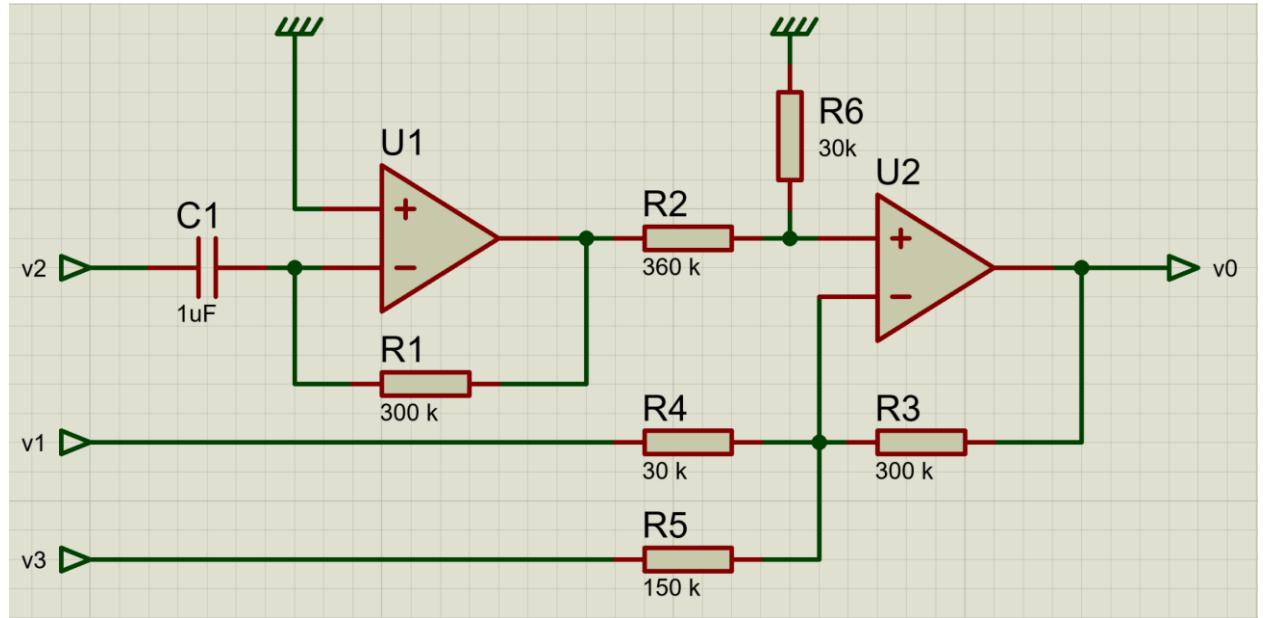


Answer on Question #79587 - Physics - Electric Circuits

Design and draw the circuit using op-amp to provide the output voltage obeying following relation of input voltages:  
 $V_0 = -10V_1 - 0.3(dV_2/dt) - 2V_3$



Answer provided by <https://www.AssignmentExpert.com>