


Answer on Question # 80096 - Physics / Electric Circuits

Question

Explain the different between the monochrome and colour television receivers with the help of appropriate block diagram.

Answer:

Basic monochrome television receiver

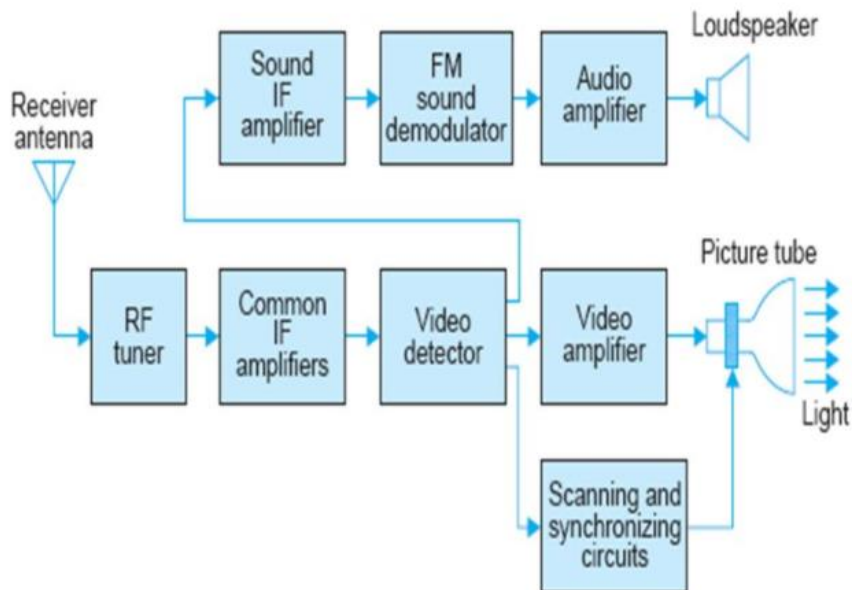

4

Colour receiver

