

Answer on Question #81726, Physics Electric Circuits


The edges of a square pyramid are made out of wires which are conductively connected at all vertices. Compute the resistance across the opposite vertices on a diagonal of the base square, given that the resistance of one meter of the wire is 1Ω , the height of the pyramid is $\sqrt{7}$ m and the base length is 2m.

Solution

1/2 the diagonal of the square is: $\frac{\sqrt{8}}{2}$

Side a square pyramid: $x = \sqrt{(\frac{\sqrt{8}}{2})^2 + \sqrt{7}^2} = 3 \text{ metres} = 3 \text{ Ohm}$

Convert the schema:

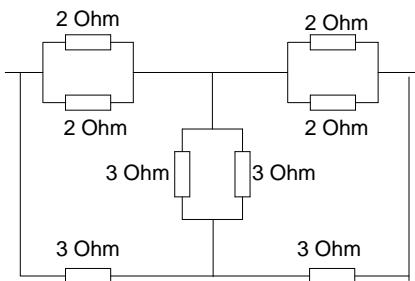

Total resistance of this circuit $R=1.5 \text{ Ohm}$

Answer: $R=1.5 \text{ Ohm}$

Answer provided by <https://www.AssignmentExpert.com>