Answer on Question #82735, Physics / Electromagnetism

Question:

Derive the equation of charging and discharging of capacitor (in context of the concept of electrostatic) when DC voltage is applied? <u>Solution:</u>

If an electrical circuit has resistor R, capacitor C and voltage source U, then $iR + \frac{q}{C} = U$; while

current $i = \frac{dq}{dt}$. Differentiating, we obtain the desirable equation: $\frac{d^2q}{dt^2} + \frac{1}{RC}\frac{dq}{dt} = 0$; it's solution is well known and for the concrete case should be added by the particular solution of the inhomogeneous equation—if any - as well as to be concretized in accordance with initial and final conditions.

The answer:

$$\frac{d^2q}{dt^2} + \frac{1}{RC}\frac{dq}{dt} = 0$$

Answer provided by https://www.AssignmentExpert.com