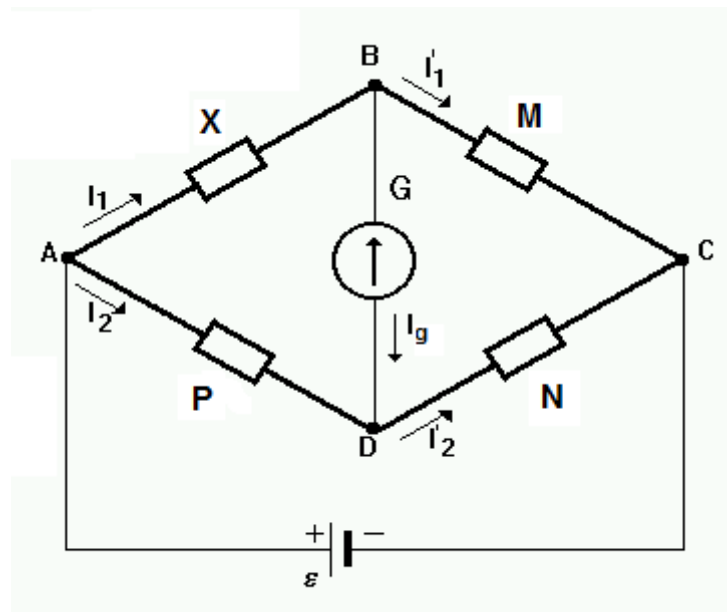


Answer on Question #85248 - Physics - Mechanics | Electric Circuits

The Wheatstone bridge. The circuit shown in Fig. P26.81. called a Wheatstone bridge, is used to determine the value of an unknown resistor X by comparison with three resistor M , N , and P whose resistances can be varied. For each setting, the resistance of each resistor is precisely known. With Switches K_1 and K_2 closed, these resistors are varied until the current in the galvanometer G is zero; the bridge is then said to be balanced. Show that under this condition the unknown resistance is given by $X=MP/N$. (This method permits very high precision in comparing resistors.) If the galvanometer G shows zero deflection when $M=850.0$ ohms, $N=15.00$ ohms and $P=33.48$ ohms, what is the unknown resistance X ?

Solution:



According to the first Kirchhoff rule for node B:

$$I_1 - I_1' - I_g = 0.$$

According to the first Kirchhoff rule for node D:

$$I_2 - I_2' + I_g = 0.$$

For balanced bridge $I_g = 0$, so:

$$I_1 = I_1',$$

$$I_2 = I_2'.$$

According to the second Kirchhoff rule for circuit ABDA:

$$I_1 X + I_g R_g - I_2 P = 0,$$

According to the second Kirchhoff rule for circuit BCDB:

$$I_1' M - I_2' N - I_g R_g = 0.$$

For balanced bridge:

$$I_1 X - I_2 P = 0,$$

$$I_1 M - I_2 N = 0.$$

Solve this system of equations:

$$I_1 = \frac{I_2 P}{X},$$

$$\frac{I_2 P}{X} M = I_2 N,$$

$$X = \frac{MP}{N} = \frac{850.00 \cdot 33.48}{15} = 1897.20 \text{ Ohm.}$$

Answer: Unknown resistance X equals 1897.20 Ohm.

Answer provided by <https://www.AssignmentExpert.com>